



Faculty of Engineering and Technology

Department of Electrical and Computer Engineering

ENCS3310

ADVANCED DIGITAL SYSTEMS DESIGN

FIRST SEMESTER PROJECT 2023-2024

Prepared by: **Lana Mahmoud Ali Musaffer**

ID: 1210455

Section: 2

Instructor: Dr. Abdallatif Abuissa

Abstract

This project aims to learn how to implement ALU and register file modules to build a simple microprocessor, so we can combine what we learned in our verilog chapter in this course. In addition, to gained a practical knowledge of module connections and working with delays and synchronization. Moreover, to learn how to run a program and test it with various cases and scenarios.

Table of Contents

Abstract	I
Table of Contents	II
Table of Figures	III
1. Theory	1
1.1 Arithmetic Logic Unit	1
1.2 Register File	2
2. Procedure and Discussion	3
2.1 Part One: Main Components	3
2.2.1 The ALU	3
2.2.2 The Register File	5
2.2 Part Two: Simple Microprocessor	7
HOW MY DESIGN WORKS	12
3. Conclusion	14
4. References	15
5. Appendix	16

Table of Figures

FIGURE 1. 1: ARITHMETIC LOGIC UNIT	1
FIGURE 1. 2: REGISTER FILE	2
FIGURE 2. 1: BASIS ALU MODULE. FIGURE 2. 2: ALU BLOCK DIAGRAM.....	3
FIGURE 2. 3: OPCODE TABLE.....	3
FIGURE 2. 4: ALU MODULE CODE	4
FIGURE 2. 5: BASIS REGFILE MODULE. FIGURE 2. 6: BLOCK DIAGRAM FOR REGFILE	5
FIGURE 2. 7: DATA TABLE	5
FIGURE 2. 8: REGFILE MODULE CODE	6
FIGURE 2. 9: BASIS OF MPTOP MODULE FIGURE 2. 10: BLOCK DIAGRAM FOR MPTOP	7
FIGURE 2. 11: MPTOP MODULE CODE	7
FIGURE 2. 12: MP_TOP MODULE CODE	11
FIGURE 2. 13: MP_TOP MODULE RESULTS	12
FIGURE 4. 1: RESULTS FOR ALU MODULE	19
FIGURE 4. 2: RESULTS FOR REG_FILE MODULE.....	21

1. Theory


A Microprocessor is an important component of a computer architecture, it is used to perform different tasks on our computers. It is a programmable device that processes input through some arithmetic and logical operations over it and produces the desired output. In simple words, “a Microprocessor is a digital device on a chip that can fetch instructions from memory, decode and execute them, and give results. It Takes a bunch of instructions in machine language and executes them, telling the processor what it has to do”.[1]

In modern microprocessor design, the ALU and register file are two critical blocks that work together to execute instructions. The ALU performs operations on data stored in the register file, and the results are then stored back in the registers. The interaction between these components forms the basis of the microprocessor's ability to execute complex machine code instructions. As technology progresses, designers continue to refine and enhance these components, optimizing their performance and contributing to the ongoing evolution of microprocessor architecture.

 1.1 Arithmetic Logic Unit

The Arithmetic Logic Unit (ALU) is a very essential component of the central processing unit (CPU), it performs arithmetic and logical operations within a computer's processor. The ALU is typically designed in such a way that it has direct input and output access to the random access memory (RAM). In modern computers, the ALU is itself is divided into two categories, Arithmetic Unit (AU), and Logic Unit (LU).

“ALU’s operations are Arithmetic Operators, which refers to bit subtraction and addition, even though it does multiplication and division. Multiplication and division processes, on the other hand, are more expensive to do. Addition can be used in place of multiplication, while subtraction can be used in place of division. **Bit-Shifting Operators**, it is responsible for a multiplication operation, which involves shifting the locations of a bit to the right or left by a particular number of places. **Logical Operations** consist of NOR, AND, NOT, NAND, XOR, OR, and more.” [2]




[3]

Figure 1. 1: Arithmetic Logic Unit

 1.2 Register File

“Registers are a type of computer memory built directly into the processor or Central Processing Unit (CPU) that is used to store and manipulate data during the execution of instructions. A register may hold an instruction, a storage address, or any kind of data (such as a bit sequence or individual characters)”. [4]

A register file is a collection of registers within a microprocessor that serves as fast, small-capacity storage locations for data. Registers are essential for temporarily holding operands and intermediate results during computations. The register file provides quick access to these data storage units, allowing the microprocessor to efficiently manage information during its operations. As technology advanced, the size and organization of register files evolved to meet the increasing demands of computing power and efficiency.



[5]

Figure 1. 2: Register File

2. Procedure and Discussion:

2.1 Part One: Main Components

2.2.1 The ALU

In this part, I built an ALU module, with two 32-bit inputs, a and b respectively, and a 32-bit output called result. This ALU module performs various logical and arithmetic operations, based on the value of the 6-bit opcode, and these operations include addition, subtraction, absolute value, inverse, maximum value, minimum value, average value, bit-wise NOT, bit-wise OR, bit-wise AND, and bit-wise XOR.

```
module alu (opcode, a, b, result );  
    input  [5:0]      opcode;  
    input  [31:0]     a, b;  
    output reg [31:0] result;  
  
endmodule
```

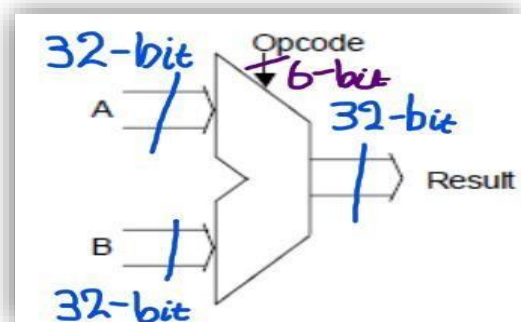


Figure 2. 1: Basis ALU Module.

Figure 2. 2: ALU Block Diagram.

My ID number is 1210455, so the last digit is 5, the below figure shows the opcodes that I used in each instruction. In my code the opcode is represented in **binary** values.

Digit of ID no.	0	1	2	3	4	5	6	7	8	9
a + b	8	6	6	4	6	3	4	4	1	5
a - b	9	8	9	11	2	15	10	14	6	8
a	2	10	1	8	5	13	3	8	13	13
-a	10	12	5	6	4	12	12	11	8	7
max(a,b)	12	14	7	13	7	7	7	10	7	3
min (a,b)	1	11	8	14	10	1	2	1	4	6
avg(a,b)	13	13	11	7	9	9	6	13	11	10
not a	5	15	14	9	13	10	13	6	15	2
a or b	4	2	13	12	8	14	14	9	3	15
a and b	11	3	12	10	1	11	11	5	5	4
a xor b	15	9	4	5	3	5	8	7	2	12

Figure 2. 3: Opcode Table.

```

1 //Lana Musaffer 1210455
2 module alu (opcode, a, b, result);
3     input [5:0] opcode;
4     input signed [31:0] a, b;
5     output reg signed [31:0] result;
6
7     always @(*)
8     begin
9         case (opcode)
10            // opcode = 3 --> a+b (addition)
11            6'b000011: result = a + b;
12
13            // opcode = 15 --> a-b (subtraction)
14            6'b001111: result = a - b;
15
16            // opcode = 13 --> |a| (the absolute value of a)
17            6'b001101: if (a < 0)
18                result = -$signed(a);
19            else
20                result = a;
21
22            // opcode = 12 --> negate the value of a
23            6'b001100: result = -$signed(a);
24
25            // opcode = 7 --> max(a, b) (the maximum of a and b)
26            6'b000111: if (a > b)
27                result = a;
28            else
29                result = b;
30
31            // opcode = 1 --> min(a, b) (the minimum of a and b)
32            6'b000001: if (a < b)
33                result = a;
34            else
35                result = b;
36
37            // opcode = 9 --> avg(a,b)
38            //(the average of a and b --> the integer part only and remainder is ignored)
39            6'b001001: result = (a + b) / 2;
40
41            // opcode = 10 --> not a
42            6'b001010: result = ~a;
43
44            // opcode = 14 --> a or b
45            6'b001110: result = (a | b);
46
47            // opcode = 11 --> a and b
48            6'b001011: result = (a & b);
49
50            // opcode = 5 --> a xor b
51            6'b000101: result = (a ^ b);
52
53            // INVALID OPCODE
54            default: begin
55                $display("INVALID OPCODE! %b", opcode);
56                result = 0;
57            end
58        endcase
59    end
60
61 endmodule
62

```

Figure 2. 4: ALU Module Code

2.2.2 The Register File

In this part, I built a very fast RAM to hold 32 x 32-bit words, with two 32-bit addresses for the read operation, addr1 and addr2 respectively, and a 32-bit address for the write operation, called addr3. This module is implemented to hold the operands that it is currently under processing.

- ✚ **Read Operation:** On the rising edge of the clock, output 1 produces the content stored at the memory location addressed by addr1, while Output 2 does the same for addr2
- ✚ **Write Operation:** the write operation utilizes the input to supply a value that is written into the memory location addressed by addr3

```
module reg_file (clk, valid_opcode, addr1, addr2, addr3, in , out1, out2);
    input          clk;
    input          valid_opcode;
    input  [4:0]    addr1, addr2, addr3;
    input  [31:0]   in;
    output reg [31:0] out1, out2;

endmodule
```

 


Figure 2. 5: Basis regFile Module.

Figure 2. 6: Block Diagram for regFile

The second-from-last digit in my ID number is 5, the below figure shows the opcodes that I used in each instruction. In my code the opcode is represented in **hexadecimal** values.

ID/ Location	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	0	0	0	0	0	0
1	7942	11662	12642	12996	4198	11930	4616	15034	5986	16302
2	13224	11562	10592	11490	5596	5348	11640	8854	12250	2994
3	15462	15330	6230	7070	14426	7308	11254	170	482	1658
4	8026	9594	8940	6026	7612	15684	6786	7226	14246	5474
5	3692	14746	8776	3322	6638	12346	6784	4480	5124	6784
6	9882	3288	9436	10344	10040	9716	12432	8928	1848	10836
7	8248	5932	3056	6734	3930	7820	13548	7302	5260	4648
8	3432	1978	4850	15834	4150	5190	13462	8922	16170	524
9	178	4912	3406	15314	6406	14702	13454	1044	4766	12200
10	2378	2380	12380	6000	5400	5630	11780	6706	4298	3286
11	8302	1926	548	12196	8572	2352	13170	258	610	14734
12	592	12726	13054	11290	16324	15424	2982	7354	1510	10998
13	7430	176	2800	13350	8840	2670	8096	3294	9794	4420
14	10572	8408	12988	2086	8258	4172	514	14740	7456	8754
15	7676	8394	956	6734	11228	4300	3600	6532	5580	3246
16	1238	13604	2194	7430	8462	4744	10870	10436	9300	9040
17	16008	10222	11914	14102	13284	1286	12528	11900	12314	8714
18	2426	7262	15864	13200	4676	8122	9860	14694	12806	12008
19	11930	10190	11832	3264	3980	4558	6166	8830	10478	1006
20	6724	8734	12346	2368	5634	8534	4520	8712	11556	6724
21	12790	12432	2192	15846	7632	13340	14436	4532	6778	12746
22	4842	8724	1840	11710	9846	6918	12136	9084	8430	5462
23	7108	5412	13996	14736	5442	11700	5134	13838	5700	11810
24	6296	11082	12054	5338	12488	10722	11958	10018	13422	7590
25	3322	2212	4434	5544	6656	3346	7688	1280	11224	4368
26	10848	6188	12152	1852	832	3300	5258	5814	1990	10358
27	14698	7056	9876	3898	4664	2386	12420	670	922	15252
28	16378	3744	8734	16252	6798	11212	3560	8832	6020	11954
29	15456	5766	8308	1048	14166	3504	1248	15186	15768	13704
30	1260	3412	3422	5642	3246	8712	8724	4512	5624	1478
31	0	0	0	0	0	0	0	0	0	0

Figure 2. 7: Data Table.

```

156 ///////////////////////////////////////////////////[REG_FILE]////////////////////////////////////
157 //Lana Musaffer 1210455
158 module reg_file (clk, valid_opcode, addr1, addr2, addr3, in , out1, out2);
159     input clk;
160     input valid_opcode;
161     input [4:0] addr1, addr2, addr3;
162     input [31:0] in;
163     output reg [31:0] out1, out2;
164
165     //INITIALE DATA
166     reg [31:0] mem [0:31] = '{32'h00000000, 32'h00002E9A, 32'h000014E4, 32'h00001C8C, 32'h00003D44, 32'h0000303A, 32'h000025F4,
167     32'h00001E8C, 32'h00001446, 32'h0000396E, 32'h000015FE, 32'h00000930, 32'h00003C40, 32'h00000A6E, 32'h0000104C,
168     32'h000010CC, 32'h00001288, 32'h00000506, 32'h00001FBA, 32'h000011CE, 32'h00002156, 32'h0000341C, 32'h00001B06,
169     32'h00002DB4, 32'h000029E2, 32'h00000D12, 32'h00000CE4, 32'h00000952, 32'h00002BCC, 32'h00000DB0, 32'h00002208,
170     32'h00000000};
171
172     //When the enable input=1 the register file will operate normally.
173     //Otherwise the register file will ignore its inputs, and will not update its outputs.
174     always@(posedge clk)
175     begin
176         if(valid_opcode)
177         begin
178             //Input is used to supply a value that is written into the location addressed by Address 3 --> Write operation
179             mem[addr3] <= in;
180
181             //Out1 produces the item within the register file that is address by Address 1 --> Read Operation
182             out1 <= mem[addr1];
183
184             //Out2 produces the item within the register file that is address by Address 2 --> Read Operation
185             out2 <= mem[addr2];
186         end
187     end
188 endmodule
189

```

Figure 2. 8: regFile Module Code.

✓ Critical remarks:

A register file is a collection of registers, each capable of storing a hexadecimal value. The enable input (**valid_opcode**) controls whether the register file should respond to, and update its outputs based on the inputs. When the valid_opcode is set to 1 (high), it indicates that the register file is allowed to operate normally. In this state, the register file will accept and process its input signals, updating the values stored in the registers accordingly, so it will operate normally, it actively reads and writes data according to the specified operations. Otherwise, the valid_opcode is set to 0 (low), it signals that the register file should ignore its inputs. In this state, the register file will not update its outputs based on any incoming data. It essentially freezes its state and does not respond to changes in input values, so it will become insensitive to changes in the input signals. The values stored in the registers remain unchanged, and the register file does not output any new data.

Another point is: [Synchronizing the register file](#) to a clock helps avoid potential problems, such as reading and overwriting occurring simultaneously. I will talk about synchronization later in detail or you can just click to move to this topic.

2.2 Part Two: Simple Microprocessor

In this part, I made machine instructions and they are represented as 32-bit numbers, in a specific format. The opcode, determining the operation to be performed, is denoted by the first 6 bits. The next 5 bits identify the first source register, the subsequent 5 bits identify the second source register, and the next 5 bits designate the destination register. The remaining 11 bits in the instruction format are unused. This structured format ensures a clear and organized representation of instructions, to get efficient decoding and execution by the processor. Then, I connected the main components, ALU and RAM, in order to integrate a simple microprocessor

```

module mp_top (clk, instruction , result );
    input          clk;
    input  [31:0]   instruction;
    output reg [31:0] result;

endmodule

```

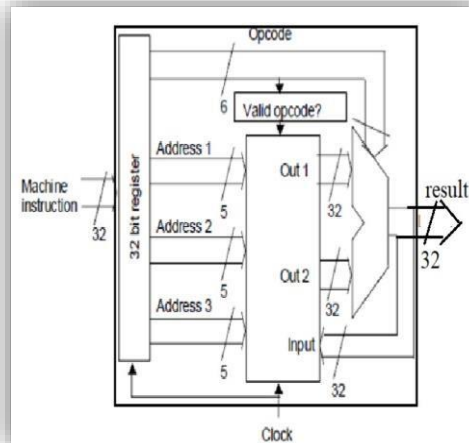


Figure 2. 9: Basis of mpTOP Module

Figure 2. 10: Block Diagram for mpTOP

```

258 ///////////////////////////////////////////////////////////////////[MP_TOP]/////////////////////////////////////////////////////////////////
259 //Lana Musaffer 1210455
260 module mp_top (clk, instruction , result );
261     input clk;
262     input [31:0] instruction;
263     output reg signed [31:0] result;
264
265     reg [5:0] opcode; //The first 6 bits identify the opcode
266     reg [4:0] addr1, addr2, addr3;
267     reg [31:0] out1, out2;
268     reg [31:0] instructionUnused;
269     reg [5:0] valid_opcode;
270
271     //Extract opcode from instruction, then check if opcode is valid
272     always @(posedge clk) begin
273         opcode = instruction[5:0];
274         valid_opcode = (opcode == 6'b000011) || (opcode == 6'b001111) || (opcode == 6'b001101) || (opcode == 6'b001100) ||
275             (opcode == 6'b000111) || (opcode == 6'b000001) || (opcode == 6'b001001) || (opcode == 6'b001010) ||
276             (opcode == 6'b001110) || (opcode == 6'b001011) || (opcode == 6'b000101);
277
278         if(valid_opcode) begin
279             addr1 = instruction[10:6]; //The next 5 bits identify first source register
280             addr2 = instruction[15:11]; //The next 5 bits identify second source register
281             addr3 = instruction[20:16]; //The next 5 bits identify destination register
282             instructionUnused = instruction; //To unused bits in instruction for later use
283             instructionUnused[31:21] = 0; //The final 11 bits are unused
284         end
285     end
286
287     reg_file Reg(clk, valid_opcode, addr1, addr2, addr3, result, out1, out2); //CONNECT THE REGISTER FILE FIRST
288
289     alu MyAlu(instruction[5:0], out1, out2, result); //CONNECT THE ALU MODULE
290 endmodule

```

Figure 2. 11: mpTOP Module Code

Test Bench For mp_top:

```

307 //Lana Musaffer 1210455
308 module mp_top_tb;
309
310     reg clk;
311     reg [31:0] instruction;
312     wire signed [31:0] result;
313
314     reg test_failed; //Flag to indicate test failure
315     reg [5:0] opcode = instruction[5:0];
316
317     //Instantiate the mp_top module
318     mp_top MP_TOP(clk, instruction, result);
319
320     //Clock generation
321     initial begin
322         clk = 0;
323         forever #5 clk = ~clk;
324     end
325
326     //task for delays
327     task DELAY;
328         #20;
329     endtask
330
331     //calculate the expected value of maximum value
332     function [31:0] maxVALUE(input [31:0] a, input [31:0] b);
333         if (a > b)
334             maxVALUE = a;
335         else
336             maxVALUE = b;
337     endfunction
338
339     //calculate the expected value of minimum value
340     function [31:0] minVALUE(input [31:0] a, input [31:0] b);
341         if (a < b)
342             minVALUE = a;
343         else
344             minVALUE = b;
345     endfunction
346
347     reg [31:0] instructions [0:14]; //Define an array of instructions
348
349     /*****ARRAY OF INSTRUCTIONS*****/
350     initial begin
351         instructions[0] = 32'b0000000000_0000_0000_100001; // INVALID OPCODE
352         instructions[1] = 32'b0000000000_1111_0000_000011; // ADDITION; RESULT = VALUE AT ADDR0 + VALUE AT ADDR1
353         instructions[2] = 32'b0000000000_0000_0000_001111; // SUBTRACTION; RESULT = VALUE AT ADDR0 - VALUE AT ADDR1
354         instructions[3] = 32'b0000000000_0000_0000_001101; // ABSOLUTE; RESULT = VALUE AT ADDR1
355         instructions[4] = 32'b0000000000_0000_0000_001100; // NEGATIVE; RESULT = - VALUE AT ADDR1
356         instructions[5] = 32'b0000000000_1111_0000_000111; // MAX; RESULT = MAX(VALUE AT ADDR0, VALUE AT ADDR1)
357         instructions[6] = 32'b0000000000_0000_0000_000111; // MIN; RESULT = MIN(VALUE AT ADDR3, VALUE AT ADDR1)
358         instructions[7] = 32'b0000000000_0000_0010_001001; // AVERAGE; RESULT = (VALUE AT ADDR4 + VALUE AT ADDR5)/2
359         instructions[8] = 32'b0000000000_0000_0000_000101; // NOT; RESULT = ~VALUE AT ADDR1
360         instructions[9] = 32'b0000000000_0000_0101_010110; // ORR; RESULT = VALUE AT ADDR10 | VALUE AT ADDR11
361         instructions[10] = 32'b0000000000_0000_0011_001101; // AND; RESULT = VALUE AT ADDR6 & VALUE AT ADDR7
362         instructions[11] = 32'b0000000000_0000_0100_010001; // XOR; RESULT = VALUE AT ADDR8 | VALUE AT ADDR9
363         instructions[12] = 32'b0000000000_0000_0000_111111; // INVALID OPCODE; RESULT = LAST RESULT
364     end
365

```

```

365
366 /*****START THE TEST*****/
367 initial begin
368     test_failed = 0; // Initialize the flag
369
370     // Iterate through all tests
371     for (int test_num = 0; test_num <= 12; test_num = test_num + 1) begin
372         instruction = instructions[test_num];
373
374         // Check for invalid opcode in Test 0
375         if (test_num == 0 && instruction[5:0] != (opcode == 6'b000011) || (opcode == 6'b001111) || (opcode == 6'b001101) ||
376             (opcode == 6'b001100) || (opcode == 6'b000111) || (opcode == 6'b000001) || (opcode == 6'b001001) ||
377             (opcode == 6'b001010) || (opcode == 6'b001110) || (opcode == 6'b001011) || (opcode == 6'b000101))
378             begin
379                 DELAY;
380                 if (result == 32'h00000000) begin
381                     $display("Test %0d FAILED!, instruction = %b, result = %h", test_num, instruction, result);
382                 end
383             end
384
385         /*****
386         // TEST CASE 0: INVALID OPCODE
387         if (test_num == 0) begin // RESULT IS NOT DEFINED
388             DELAY;
389             if (instruction[5:0] == 6'b100001) begin
390                 $display("Test 0 FAILED! instruction= %b, result = %h", instruction, result);
391                 test_failed = 0; // Set the flag to indicate failure
392             end
393         end
394         *****/

```

```

394 /*****
395 //TEST CASE 1: ADDITION --> OPCODE = 3
396 if (test_num == 1) begin
397     DELAY;
398     if (result != (32'h00002E9A + 32'h00000000)) begin
399         $display("Test 1 FAILED! Expected: %h, Got: %h", (32'h00002E9A + 32'h00000000), result);
400         test_failed = 1; // Set the flag to indicate failure
401     end else begin
402         $display("Test 1 PASSED!, instruction= %b, result = %h", instruction, result);
403     end
404 end
405
406 /*****
407
408 //TEST CASE 2: SUBTRACTION --> OPCODE = 15
409 if (test_num == 2) begin
410     DELAY;
411     if (result != (32'h00000000 - 32'h00002E9A)) begin
412         $display("Test 2 FAILED! Expected: %h, Got: %h", (32'h00000000 - 32'h00002E9A), result);
413         test_failed = 1; // Set the flag to indicate failure
414     end else begin $display("Test 2 PASSED!, instruction= %b, result = %h", instruction, result);
415     end
416 end
417 /*****
418
419 //TEST CASE 3: ABSOLUTE --> OPCODE = 13
420 if (test_num == 3) begin
421     DELAY;
422     if (result != (32'h00002E9A)) begin
423         $display("Test 3 FAILED! Expected: %h, Got: %h", (32'h00002E9A), result);
424         test_failed = 1; // Set the flag to indicate failure
425     end else begin $display("Test 3 PASSED!, instruction= %b, result = %h", instruction, result);
426     end
427 end
428 /*****

```



```

428 //*****
429
430 //TEST CASE 4: NEGATIVE --> OPCODE = 12
431 if (test_num == 4) begin
432     DELAY;
433     if (result != -$signed(32'h00002E9A)) begin
434         $display("Test 4 FAILED! Expected: %h, Got: %h", -$signed(32'h00002E9A), result);
435         test_failed = 1; // Set the flag to indicate failure
436     end else begin $display("Test 4 PASSED!, instruction= %b, result = %h", instruction, result);
437     end
438 end
439 //*****
440
441 //TEST CASE 5: MAX --> OPCODE = 7
442 if (test_num == 5) begin
443     DELAY;
444     if (result != maxVALUE(32'h00002E9A, 32'h00000000)) begin
445         $display("Test 5 FAILED! Expected: %h, Got: %h", maxVALUE(32'h00002E9A, 32'h00000000), result);
446         test_failed = 1; // Set the flag to indicate failure
447     end else begin $display("Test 5 PASSED!, instruction = %b, result = %h", instruction, result);
448     end
449 end
450 //*****
451
452 //TEST CASE 6: MIN --> OPCODE = 1
453 if (test_num == 6) begin
454     DELAY;
455     if (result != minVALUE(32'h00002E9A, 32'h00001C8C)) begin
456         $display("Test 6 FAILED! Expected: %h, Got: %h", minVALUE(32'h00002E9A, 32'h00001C8C), result);
457         test_failed = 1; // Set the flag to indicate failure
458     end else begin $display("Test 6 PASSED!, instruction= %b, result = %h", instruction, result);
459     end
460 end
461 //*****
462
463 //TEST CASE 7: AVERAGE --> OPCODE = 9
464 if (test_num == 7) begin
465     DELAY;
466     if (result != ((32'h00003D44 + 32'h0000303A)/32'h00000002)) begin
467         $display("Test 7 FAILED! Expected: %h, Got: %h", ((32'h00003D44 + 32'h0000303A)/32'h00000002), result);
468         test_failed = 1; // Set the flag to indicate failure
469     end else begin $display("Test 7 PASSED!, instruction= %b, result = %h", instruction, result);
470     end
471 end
472 //*****
473
474 //TEST CASE 8: NOT --> OPCODE = 10
475 if (test_num == 8) begin
476     DELAY;
477     if (result != ~(32'h00002E9A)) begin
478         $display("Test 8 FAILED! Expected: %h, Got: %h", ~(32'h00002E9A), result);
479         test_failed = 1; // Set the flag to indicate failure
480     end else begin $display("Test 8 PASSED!, instruction= %b, result = %h", instruction, result);
481     end
482 end
483 //*****
484
485 //TEST CASE 9: ORR --> OPCODE = 14
486 if (test_num == 9) begin
487     DELAY;
488     if (result != (32'h000015FE | 32'h00000930)) begin
489         $display("Test 9 FAILED! Expected: %h, Got: %h", (32'h000015FE | 32'h00000930), result);
490         test_failed = 1; // Set the flag to indicate failure
491     end else begin $display("Test 9 PASSED!, instruction= %b, result = %h", instruction, result);
492     end
493 end
494 //*****

```

```

494  /*****
495
496  //TEST CASE 10: AND --> OPCODE = 11
497  if (test_num == 10) begin
498      DELAY;
499      if (result != (32'h000025F4 & 32'h00001E8C)) begin
500          $display("Test 10 FAILED! Expected: %h, Got: %h", (32'h000025F4 & 32'h00001E8C), result);
501          test_failed = 1; // Set the flag to indicate failure
502      end else begin $display("Test 10 PASSED!, instruction= %b, result = %h", instruction, result);
503      end
504  end
505  /*****
506
507  //TEST CASE 11: XOR --> OPCODE = 5
508  if (test_num == 11) begin
509      DELAY;
510      if (result != (32'h00001446 ^ 32'h0000396E)) begin
511          $display("Test 11 FAILED! Expected: %h, Got: %h", (32'h00001446 ^ 32'h0000396E), result);
512          test_failed = 1; // Set the flag to indicate failure
513      end else begin $display("Test 11 PASSED!, instruction= %b, result = %h", instruction, result);
514      end
515  end
516  /*****
517
518  // TEST CASE 12: INVALID OPCODE
519  if (test_num == 12) begin
520      DELAY;
521      if (instruction[5:0] == 6'b111111) begin
522          $display("Test 12 FAILED! instruction= %b, result = %h", instruction, result);
523          test_failed = 0; // Set the flag to indicate failure
524      end
525  end
526  /*****
527  end
528
529  //Check if any test failed
530  if (test_failed == 1) begin
531      $display("SIMULATION PASSED: ALL TESTS PASSED");
532  end else begin
533      $display("SIMULATION FAILED: SOME TESTS DID NOT PASS");
534  end
535
536  //FINISH SIMULATION
537  #10 $finish;
538  end
539
540  endmodule
541

```

Activate W

Figure 2. 12: mp_top Module Code.

HOW MY DESIGN WORKS:


In my designed microprocessor system, the relationship between the clock cycle and instruction execution is crucial for synchronous operation. The clock (CLK) acts as a synchronization mechanism, and the processor responds to the rising edge of the clock. On each rising edge, the processor decodes machine instructions, extracting the opcode and relevant addresses. The subsequent actions, such as enabling the register file and processing operands in the ALU module. In the first cycle, it takes the instruction, and in the second one, it makes the operations.

Notably, the result of an instruction is written to the register file on the same rising edge of the clock. This ensures that the register file is updated synchronously with the instruction execution. The synchronous design guarantees consistency and predictability in the state of the processor at each clock cycle. Therefore, the relationship between the clock cycle and the result being written to the register is immediate, allowing for precise control over the processor's behavior.

For testing, I initialized a flag to keep track of the pass or fail cases, and I made the delay in a task to make it easier for me when changing it to the desired value just ONCE, also I calculated the expected values of the max and min in a function for better readability. I created an array of instructions and ensured the representation for each provided opcode. During testing, I printed both the input instruction and the corresponding output result for thorough examination. In addition, for every instruction, I computed the expected result and compared it with the actual output. If any instruction failed to produce the expected outcome, the test was marked as unsuccessful; otherwise, it was taken as a success.

RESULTS OVERVIEW:

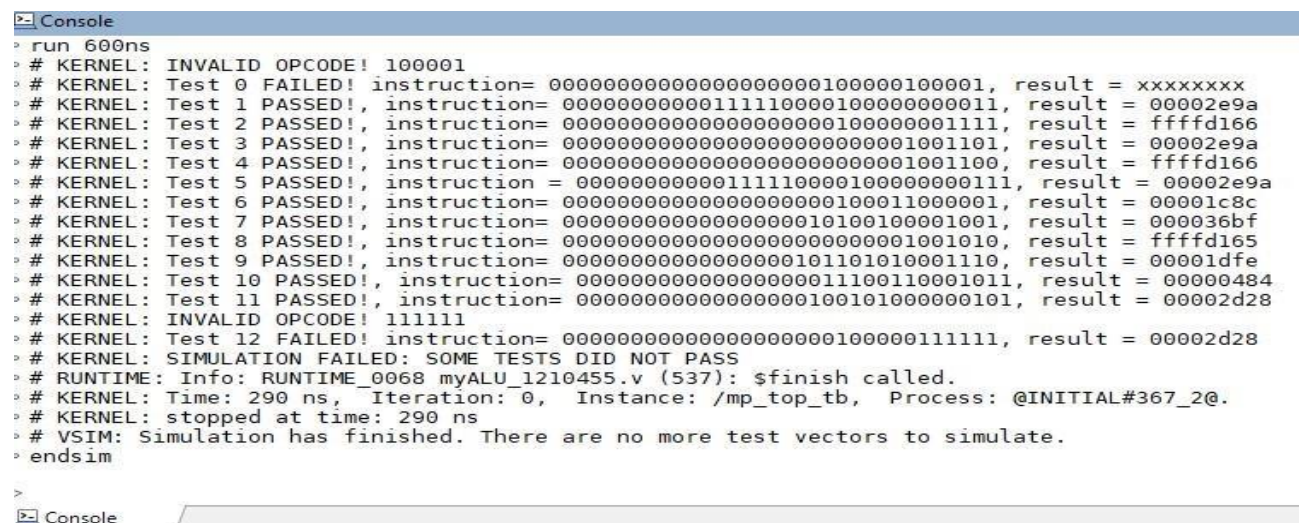Note that I showed in details (in the code) each instruction how it is calculated and also the expected value.



```
> run 600ns
# KERNEL: INVALID OPCODE! 100001
# KERNEL: Test 0 FAILED! instruction= 000000000000000000000000100000100001, result = xxxxxxxx
# KERNEL: Test 1 PASSED! instruction= 00000000000111110000100000000011, result = 00002e9a
# KERNEL: Test 2 PASSED! instruction= 000000000000000000000000100000001111, result = ffffd166
# KERNEL: Test 3 PASSED! instruction= 00000000000000000000000000001001101, result = 00002e9a
# KERNEL: Test 4 PASSED! instruction= 000000000000000000000000000000001001100, result = ffffd166
# KERNEL: Test 5 PASSED! instruction= 000000000001111100001000000000111, result = 00002e9a
# KERNEL: Test 6 PASSED! instruction= 000000000000000000000000100011000001, result = 00001c8c
# KERNEL: Test 7 PASSED! instruction= 00000000000000000000000010100100001001, result = 000036bf
# KERNEL: Test 8 PASSED! instruction= 000000000000000000000000000000001001010, result = ffffd165
# KERNEL: Test 9 PASSED! instruction= 000000000000000000000000101101010001110, result = 00001dfe
# KERNEL: Test 10 PASSED! instruction= 00000000000000000000000011100110001011, result = 00000484
# KERNEL: Test 11 PASSED! instruction= 000000000000000000000000100101000000101, result = 00002d28
# KERNEL: INVALID OPCODE! 111111
# KERNEL: Test 12 FAILED! instruction= 000000000000000000000000100000111111, result = 00002d28
# KERNEL: SIMULATION FAILED: SOME TESTS DID NOT PASS
# RUNTIME: Info: RUNTIME_0068 myALU_1210455.v (537): $finish called.
# KERNEL: Time: 290 ns, Iteration: 0, Instance: /mp_top_tb, Process: @INITIAL#367_2@.
# KERNEL: stopped at time: 290 ns
# VSIM: Simulation has finished. There are no more test vectors to simulate.
endsim
```

Figure 2. 13: mp_top Module Results.

CHALLENGES & AMBITIONS

```
instructions[1] = 32'b000000000000_11111_00001_00000_000011;
```

```
// ADDITION; RESULT = VALUE AT ADDR0 + VALUE AT ADDR1
```

```
instructions[2] = 32'b000000000000_00000_00001_11111_001111;
```

```
// SUBTRACTION; RESULT = VALUE AT ADDR32 - VALUE AT ADDR1
```

- When I tried to test this case to make sure that my code worked perfectly and it wrote back the result at each clock cycle, but unfortunately, it didn't work as it was supposed to be; VALUE AT ADDR32 → Result from the addition operation, instead it just contained the original data.
- I think this issue is because of the delay, and I tried to solve it by using buffer and DFF, but both of them didn't work):
- This is the only problem that I have in my code.

3. Conclusion:

In conclusion, the design and implementation of the microprocessor system involved the creation of two main components, the Arithmetic Logic Unit (ALU) and the Register File. These components function in synchrony within the microprocessor, responding to the rising edge of the clock during each clock cycle. The ALU performs arithmetic and logical operations based on machine instructions, while the Register File manages the storage of the data. During testing, a thorough approach was taken to evaluate the processor's correctness and reliability. The test bench covered various opcodes, with careful examination of each instruction's input and output. So, a very fast and efficient microprocessor is built.

4. References:

- [1] [Introduction of Microprocessor - GeeksforGeeks](#)
- [2] [ALU \(Arithmetic Logic Unit\) | GATE Notes \(byjus.com\)](#)
- [3] <https://www.google.com/url?sa=i&url=https%3A%2F%2Fati.ttu.ee%2FAY0340%2Fflabs%2FTutorials%2FSystemC%2FALU.html&psig=AOvVaw0jYyRuJlOG2vNgi0p4RiHU&ust=1705173394640000&source=images&cd=vfe&opi=89978449&ved=0CBMQjRxqFwoTCPito4jI2IMDFQAAAAAdAAAAABAD>
- [4] [https://www.google.com/url?sa=t&rct=j&q=&esrc=s&source=web&cd=&cad=rja&uact=8&ved=2ahUKEwi48YDfm-KDaxUyUKQEHTdRAOAQFnoECBIQAw&url=https%3A%2F%2Fwww.totalphase.com%2Fblog%2F2023%2F05%2Fwhat-is-register-in-cpu-how-does-it-work%2F%23%3A~%3Atext%3DRegisters%2520are%2520a%2520type%2520of%2Cbit%2520sequence%2520or%2520individual%2520characters\).&usq=AOvVaw3z_zC6FXtRMhrJw79a7Qte&opi=89978449](https://www.google.com/url?sa=t&rct=j&q=&esrc=s&source=web&cd=&cad=rja&uact=8&ved=2ahUKEwi48YDfm-KDaxUyUKQEHTdRAOAQFnoECBIQAw&url=https%3A%2F%2Fwww.totalphase.com%2Fblog%2F2023%2F05%2Fwhat-is-register-in-cpu-how-does-it-work%2F%23%3A~%3Atext%3DRegisters%2520are%2520a%2520type%2520of%2Cbit%2520sequence%2520or%2520individual%2520characters).&usq=AOvVaw3z_zC6FXtRMhrJw79a7Qte&opi=89978449)
- [5] https://www.google.com/url?sa=i&url=http%3A%2F%2Fwww.ee.ic.ac.uk%2Fpcheung%2Fteaching%2Fee2_digital%2FLecture%252013%2520-%2520FPGA%2520Embedded%2520Memory.pdf&psig=AOvVaw0BtvGNSx14YYP-NHhAAW_&ust=1705504575536000&source=images&cd=vfe&opi=89978449&ved=0CBMQjRxqFwoTCNjhreaZ4oMDFQAAAAAdAAAAABAH

5. Appendix:

Code Snippet 1: Test Bench for ALU Module

```
`timescale 1ns/1ns

module alu_tb;

    reg [5:0] opcode;

    reg signed [31:0] a, b;

    wire signed [31:0] result;

    alu ALU(opcode, a, b, result);

    reg clk = 0;

    always #5 clk = ~clk;

    initial begin

        $monitor("TIME=%0t OPCODE=%b A=%d B=%d RESULT=%d", $time, opcode, a, b, result);

        // ADDITION TEST

        opcode = 6'b000011;

        a = 10;

        b = 5;

        #10;

        // SUBTRACTION TEST

        opcode = 6'b001111;

        a = -20;
```

```
b = 8;

#10;


// ABSOLUTE TEST

opcode = 6'b001101;

a = -15;

b = 0;

#10;


// INVERSE TEST

opcode = 6'b001100;

a = -15;

b = 0;

#10;


// MAX TEST

opcode = 6'b000111;

a = 4;

b = -9;

#10;


// MIN TEST

opcode = 6'b000001;

a = 8;

b = -4;

#10;
```

```
// AVERAGE TEST
```

```
opcode = 6'b001001;
```

```
a = 7;
```

```
b = 7;
```

```
#10;
```

```
// BIT-WISE NOT TEST
```

```
opcode = 6'b001010;
```

```
a = 7;
```

```
b = 0;
```

```
#10;
```

```
// BIT-WISE OR TEST
```

```
opcode = 6'b001110;
```

```
a = 5;
```

```
b = 4;
```

```
#10;
```

```
// BIT-WISE AND TEST
```

```
opcode = 6'b001011;
```

```
a = 5;
```

```
b = 4;
```

```
#10;
```

```
// BIT-WISE XOR TEST
```

```
opcode = 6'b000101;
```

```
a = 5;
```

```

b = 4;

#10;

// INVALID TEST

opcode = 6'b111111;

a = 0;

b = 0;

#10;

$finish;

end

endmodule

```

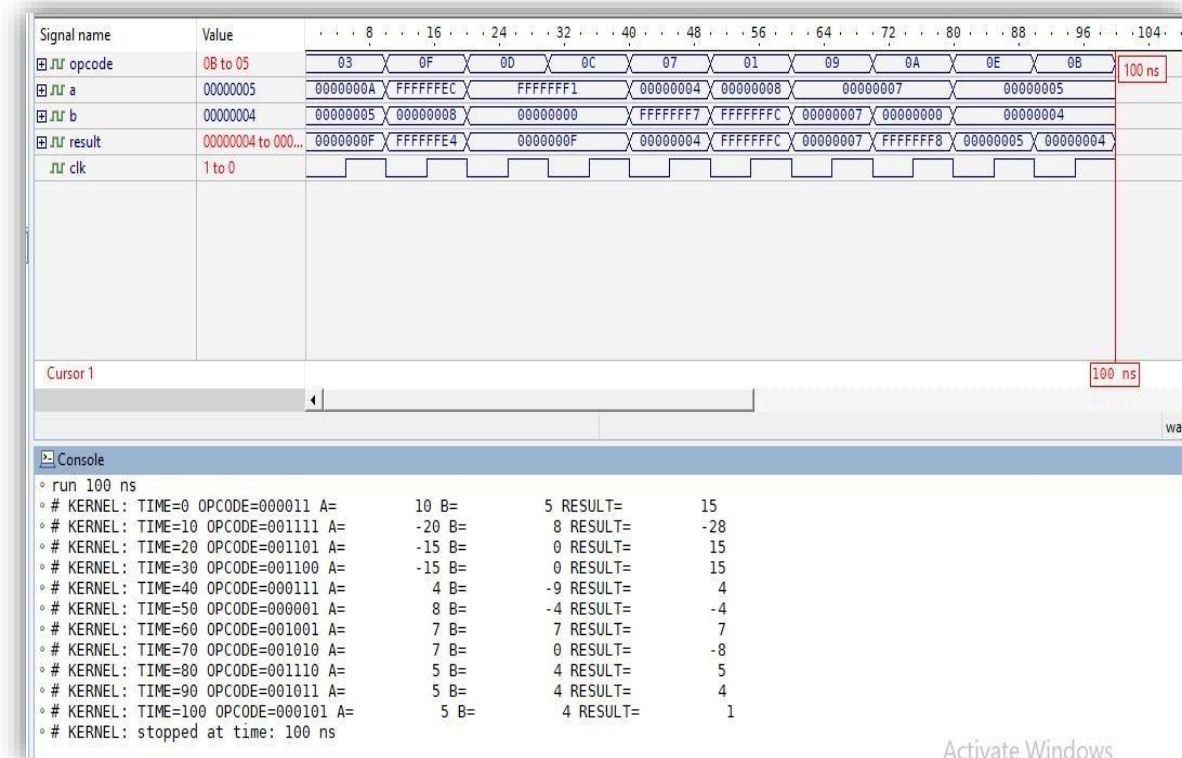


Figure 4. 1: Results for ALU module.

Code Snippet 2: Test Bench for Register File Module

```
`timescale 1ns/1ns

module regFile_tb;

reg clk;
reg valid_opcode;
reg [4:0] addr1, addr2, addr3;
reg [31:0] in;
wire [31:0] out1, out2;

reg_file RF(clk, valid_opcode, addr1, addr2, addr3, in, out1, out2);

// Clock generation
initial begin
    clk = 0;
    forever #5 clk = ~clk;
end

//      Test
initial begin
    // Test Case 1: Read operation with valid_opcode
    valid_opcode = 1;
    addr1 = 5'b00100; // address 4
    addr2 = 5'b01000; // address 8
    #10;
    if (valid_opcode)
        $display("Test Case 1: out1 = %h, out2 = %h", out1, out2); //out1=value at
address 4, out2=value at address 8
    else
        $display("Test Case 1: Invalid opcode");

    // Test Case 2: Write operation with valid_opcode
    valid_opcode = 1;
    addr3 = 5'b01100; // address 12
    in = 32'h0000000A;
    #10;
    if (valid_opcode)
        $display("Test Case 2: DATA = %h", in); //in=data written in address 12
    else
        $display("Test Case 2: Invalid opcode");

    // Test Case 3: Read operation with invalid_opcode
    valid_opcode = 0;
    addr1 = 5'b00110; // address 6
    addr2 = 5'b01010; // address 10
    #10;
    if (valid_opcode)
        $display("INVALID OPCODE");
    else
```



```

        $display("Test Case 3: Invalid opcode");

// Test Case 4: Write operation with invalid_opcode
valid_opcode = 0;
addr3 = 5'b01111; // address 15
in = 32'h000000AA;
#10;
if (valid_opcode)
    $display("INVALID OPCODE");
else
    $display("Test Case 4: Invalid opcode");

// Finish the simulation
#10 $finish;
end

endmodule

```

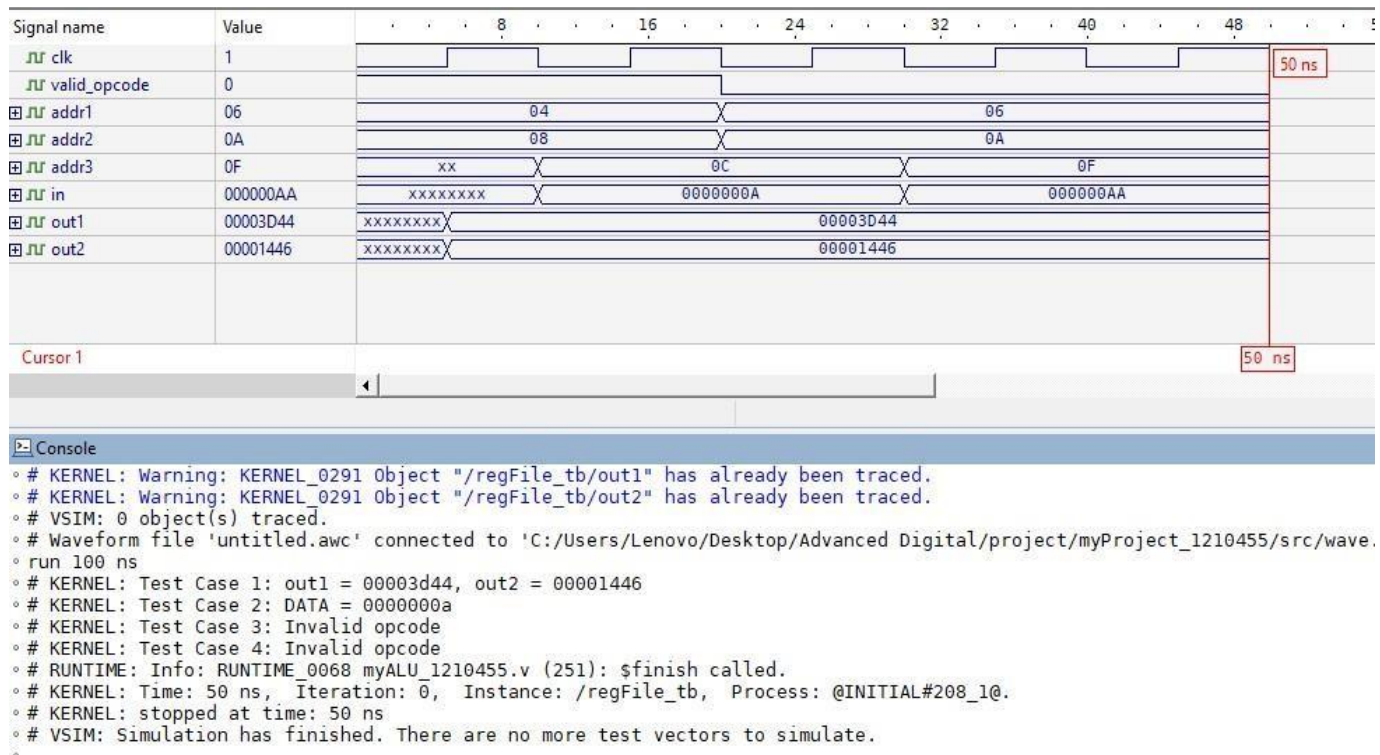


Figure 4. 2: Results for reg_file Module